

EXPERIMENT- 6


Control Path Modelling and Design

Objective:


To understand the concepts related to FSM (Moore/Mealy machine) and design the controller for a robot with the given specifications. Write the Verilog Programs for the same using any modeling style.

 Exercise Problems

- A Line follower Robot uses 2 Infra-Red (IR) sensors to detect the colour of the surface. Sensor output is High when white surface is detected and Low on a black surface. Try to model the Robot controller and then implement its hardware?**



State Diagram

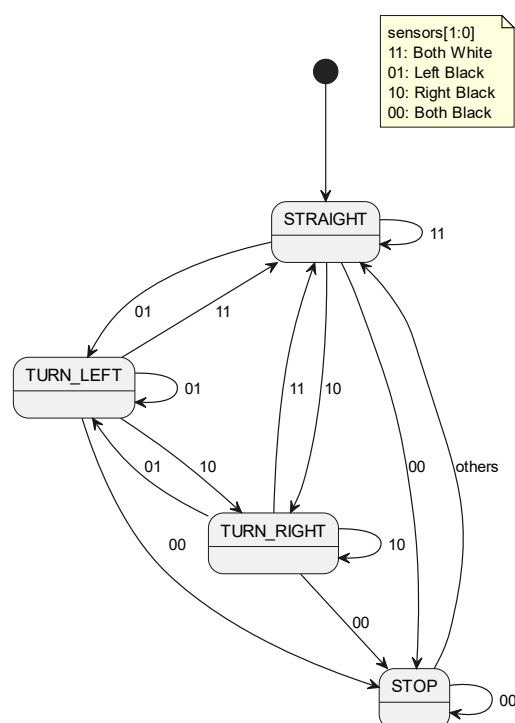

Source Code

```
module linefollower (  
    input wire clk, reset,  
    input wire sensorLeft,sensorRight,// 1:White surface, 0:Black surface  
    output reg motorLeft, motorRight  
);  
parameter [3:0]  
    STRAIGHT    = 4'b0001,  
    TURN_LEFT   = 4'b0010,  
    TURN_RIGHT  = 4'b0100,  
    STOP        = 4'b1000;  
  
    reg [3:0] current_state, next_state;  
    wire [1:0] sensors;  
    assign sensors = {sensorLeft, sensorRight};  
    always @(posedge clk or posedge reset) begin  
        if (reset)  
            current_state <= STRAIGHT;  
        else  
            current_state <= next_state;  
    end  
    always @(*) begin  
        case (current_state)  
            STRAIGHT: begin  
                case (sensors)  
                    2'b11: next_state = STRAIGHT;  
                    2'b01: next_state = TURN_LEFT;  
                    2'b10: next_state = TURN_RIGHT;  
                    2'b00: next_state = STOP;  
                    default: next_state = STRAIGHT;  
                endcase  
            end  
            TURN_LEFT: begin  
                case (sensors)  
                    2'b01: next_state = TURN_LEFT;  
                    2'b10: next_state = TURN_RIGHT;  
                    2'b11: next_state = STRAIGHT;  
                    2'b00: next_state = STOP;  
                    default: next_state = TURN_LEFT;  
                endcase  
            end  
        end  
    end
```

```

    TURN_RIGHT: begin
        case (sensors)
            2'b10: next_state = TURN_RIGHT;
            2'b01: next_state = TURN_LEFT;
            2'b11: next_state = STRAIGHT;
            2'b00: next_state = STOP;
            default: next_state = TURN_RIGHT;
        endcase
    end
    STOP: begin
        next_state = (sensors == 2'b00) ? STOP : STRAIGHT;
    end
    default: begin
        next_state = STRAIGHT;
    end
endcase
end
always @(*) begin
    case (current_state)
        STRAIGHT: {motorLeft, motorRight} = 2'b11;
        TURN_LEFT: {motorLeft, motorRight} = 2'b01;
        TURN_RIGHT: {motorLeft, motorRight} = 2'b10;
        STOP: {motorLeft, motorRight} = 2'b00;
        default: {motorLeft, motorRight} = 2'b11;
    endcase
end
endmodule

```

Testbench

```

module tb();
    reg clk, reset;
    reg sensorLeft, sensorRight;
    wire motorLeft, motorRight;
    linefollower uut ( .clk(clk),
                      .reset(reset),
                      .sensorLeft(sensorLeft),
                      .sensorRight(sensorRight),
                      .motorLeft(motorLeft),
                      .motorRight(motorRight)
                    );


```

```

always #5 clk = ~clk;
initial begin
$monitor($time," | clk = %b | reset = %b | sensorLeft = %b | sensorRight
= %b | motorLeft = %b | motorRight = %b",
clk,reset,sensorLeft,sensorRight,motorLeft,motorRight);
    clk=0;
    reset = 0;
    sensorLeft = 0;
    sensorRight = 0;
    reset = 1; #10;
    reset = 0;
    sensorLeft = 1;
    sensorRight = 1; #10; // Both sensors detect white
    sensorLeft = 0;
    sensorRight = 1; #10; // Left sensor detects black
    sensorLeft = 1;
    sensorRight = 0;#10; // Right sensor detects black
    sensorLeft = 0;
    sensorRight = 0;#10; // Both sensors detect black
    #60;
    $finish;
end
endmodule

```

Waveform

 


Console

```


ncsim>
ncsim> source /home/install/INCISIVE152/tools/inca/files/ncsimrc
ncsim> run
      0 | clk = 0 | reset = 1 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 1 | motorRight = 1
      5 | clk = 1 | reset = 1 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 1 | motorRight = 1
     10 | clk = 0 | reset = 0 | sensorLeft = 1 | sensorRight = 1 | motorLeft = 1 | motorRight = 1
     15 | clk = 1 | reset = 0 | sensorLeft = 1 | sensorRight = 1 | motorLeft = 1 | motorRight = 1
     20 | clk = 0 | reset = 0 | sensorLeft = 0 | sensorRight = 1 | motorLeft = 1 | motorRight = 1
     25 | clk = 1 | reset = 0 | sensorLeft = 0 | sensorRight = 1 | motorLeft = 0 | motorRight = 1
     30 | clk = 0 | reset = 0 | sensorLeft = 1 | sensorRight = 0 | motorLeft = 0 | motorRight = 1
     35 | clk = 1 | reset = 0 | sensorLeft = 1 | sensorRight = 0 | motorLeft = 1 | motorRight = 0
     40 | clk = 0 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 1 | motorRight = 0
     45 | clk = 1 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
     50 | clk = 0 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
     55 | clk = 1 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
     60 | clk = 0 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
     65 | clk = 1 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
     70 | clk = 0 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
     75 | clk = 1 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
     80 | clk = 0 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
     85 | clk = 1 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
     90 | clk = 0 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
     95 | clk = 1 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
    100 | clk = 0 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
    105 | clk = 1 | reset = 0 | sensorLeft = 0 | sensorRight = 0 | motorLeft = 0 | motorRight = 0
Simulation complete via $finish(1) at time 110 NS + 0
./linefollower_tb.v:31 $finish; \r
ncsim>

```

Schematic

 

 2. Model and implement an Elevator control system handling 4 floors (0 to 3)



Source Code

```

module elevator(
    input clk,
    input reset,
    input [1:0] current_floor,
    input [3:0] buttons_in,
    input [3:0] buttons_out,
    output reg [3:0] motor,
    output reg dir_up,
    output reg dir_down
);
    reg [3:0] floor_requests;
    reg [1:0] next_floor;
    always @(posedge clk or posedge reset)
    begin
        if (reset)
        begin
            motor <= 4'b0000;
            dir_up <= 1'b0;
            dir_down <= 1'b0;
            next_floor <= current_floor;
            floor_requests <= 4'b0000;
        end
    else

```

```
begin
    floor_requests <= buttons_in | buttons_out;
    if (floor_requests[current_floor])
    begin
        motor <= 4'b0000; // Stop at current floor
        dir_up <= 1'b0;
        dir_down <= 1'b0;
    end
    else
    begin
        if (current_floor == 2'b00 && floor_requests[1])
        begin
            next_floor <= 2'b01;
            motor <= 4'b0010;
            dir_up <= 1'b1;
            dir_down <= 1'b0;
        end
        else if (current_floor <= 2'b01 && floor_requests[2])
        begin
            next_floor <= 2'b10;
            motor <= 4'b0100;
            dir_up <= 1'b1;
            dir_down <= 1'b0;
        end
        else if (current_floor <= 2'b10 && floor_requests[3])
        begin
            next_floor <= 2'b11;
            motor <= 4'b1000;
            dir_up <= 1'b1;
            dir_down <= 1'b0;
        end
        else if (current_floor >= 2'b01 && floor_requests[0])
        begin
            next_floor <= 2'b00;
            motor <= 4'b0001;
            dir_up <= 1'b0;
            dir_down <= 1'b1;
        end
        else if (current_floor >= 2'b10 && floor_requests[1])
        begin
            next_floor <= 2'b01;
            motor <= 4'b0010;
```

```
        dir_up <= 1'b0;
        dir_down <= 1'b1;
    end
    else if (current_floor >= 2'b11 && floor_requests[2])
    begin
        next_floor <= 2'b10;
        motor <= 4'b0100;
        dir_up <= 1'b0;
        dir_down <= 1'b1;
    end
    else
    begin
        motor <= 4'b0000; // No movement if no requests in any
direction
        dir_up <= 1'b0;
        dir_down <= 1'b0;
    end
end
end
end
end
endmodule
```

Testbench

```
module tb();
    reg clk;
    reg reset;
    reg [1:0] current_floor;
    reg [3:0] buttons_in;
    reg [3:0] buttons_out;
    wire [3:0] motor;
    wire dir_up;
    wire dir_down;

    elevator uut (
        .clk(clk),
        .reset(reset),
        .current_floor(current_floor),
        .buttons_in(buttons_in),
        .buttons_out(buttons_out),
        .motor(motor),
```

```
        .dir_up(dir_up),
        .dir_down(dir_down)
    );

    always #5 clk = ~clk;

    initial begin
$monitor($time," |Floor=%d | Buttons In=%b | Buttons Out=%b | Motor=%b |
Dir_Up=%b | Dir_Down=%b", current_floor, buttons_in, buttons_out, motor,
dir_up, dir_down);
        clk = 0;
        reset = 1;
        current_floor = 2'b00;
        buttons_in = 4'b0000;
        buttons_out = 4'b0000;
        #10;
        reset = 0;
        // Request to go to the 3rd floor (external)
        #10;
        buttons_out = 4'b1000; // Request for 3rd floor
        #20;
        current_floor = 2'b01; // Move to 1st floor
        #20;
        current_floor = 2'b10; // Move to 2nd floor
        #20;
        current_floor = 2'b11; // Reach 3rd floor
        #20;
        buttons_out = 4'b0000; // Clear requests

        // Request from 1st and 2nd floors (internal)
        #10;
        buttons_in = 4'b0110; // Requests for 1st and 2nd floors
        #20;
        current_floor = 2'b10; // Move to 2nd floor
        #20;
        buttons_in = 4'b0000; // Clear requests

        // Request to go down to ground floor (external)
        #10;
        buttons_out = 4'b0001; // Request for ground floor
        #20;
```




```

current_floor = 2'b10; // Move to 2nd floor
#20;
current_floor = 2'b01; // Move to 1st floor
#20;
current_floor = 2'b00; // Reach ground floor
#20;
buttons_out = 4'b0000; // Clear requests
$finish;
end
endmodule

```

Waveform

 


Console

```


ncsim>
ncsim> source /home/install/INCISIVE152/tools/inca/files/ncsimrc
ncsim> database -open waves -into waves.shm -default
ncsim> probe -create -shm tb.buttons_in tb.buttons_out tb.clk tb.current_floor tb.dir_down tb.dir_up tb.motor tb.reset
Created default SHM database waves
ncsim> Created probe 1
ncsim> run
0 |Floor=0 | Buttons In=0000 | Buttons Out=0000 | Motor=0000 | Dir_Up=0 | Dir_Down=0
20 |Floor=0 | Buttons In=0000 | Buttons Out=1000 | Motor=0000 | Dir_Up=0 | Dir_Down=0
35 |Floor=0 | Buttons In=0000 | Buttons Out=1000 | Motor=1000 | Dir_Up=1 | Dir_Down=0
40 |Floor=1 | Buttons In=0000 | Buttons Out=1000 | Motor=1000 | Dir_Up=1 | Dir_Down=0
60 |Floor=2 | Buttons In=0000 | Buttons Out=1000 | Motor=1000 | Dir_Up=1 | Dir_Down=0
80 |Floor=3 | Buttons In=0000 | Buttons Out=1000 | Motor=1000 | Dir_Up=1 | Dir_Down=0
85 |Floor=3 | Buttons In=0000 | Buttons Out=1000 | Motor=0000 | Dir_Up=0 | Dir_Down=0
100 |Floor=3 | Buttons In=0000 | Buttons Out=0000 | Motor=0000 | Dir_Up=0 | Dir_Down=0
110 |Floor=3 | Buttons In=0110 | Buttons Out=0000 | Motor=0000 | Dir_Up=0 | Dir_Down=0
125 |Floor=3 | Buttons In=0110 | Buttons Out=0000 | Motor=0010 | Dir_Up=0 | Dir_Down=1
130 |Floor=2 | Buttons In=0110 | Buttons Out=0000 | Motor=0010 | Dir_Up=0 | Dir_Down=1
135 |Floor=2 | Buttons In=0110 | Buttons Out=0000 | Motor=0000 | Dir_Up=0 | Dir_Down=0
150 |Floor=2 | Buttons In=0000 | Buttons Out=0000 | Motor=0000 | Dir_Up=0 | Dir_Down=0
160 |Floor=2 | Buttons In=0000 | Buttons Out=0001 | Motor=0000 | Dir_Up=0 | Dir_Down=0
175 |Floor=2 | Buttons In=0000 | Buttons Out=0001 | Motor=0001 | Dir_Up=0 | Dir_Down=1
200 |Floor=1 | Buttons In=0000 | Buttons Out=0001 | Motor=0001 | Dir_Up=0 | Dir_Down=1
220 |Floor=0 | Buttons In=0000 | Buttons Out=0001 | Motor=0001 | Dir_Up=0 | Dir_Down=1
225 |Floor=0 | Buttons In=0000 | Buttons Out=0001 | Motor=0000 | Dir_Up=0 | Dir_Down=0
Simulation complete via $finish(1) at time 240 NS + 0
./elevator_tb.v:66 $finish;\r
ncsim>

```

Schematic

 

 3. Design the control flow and control signals required to configure this programmable data path given in the figure to perform Exponentiation function.




Pseudocode

```

e = 1;
while (b >= 1) {
    e = e * a;
    b = b - 1;
}

```

State Diagram

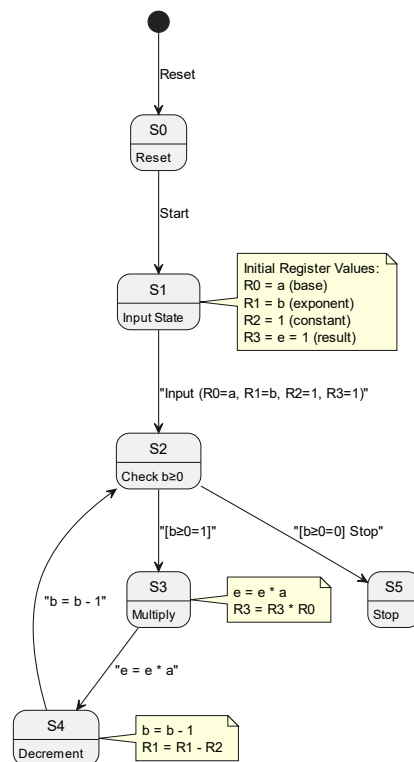

Control Signal

State	a_sel	b_sel	op_sel	wsel	wen
S0	10	10	10	1	1
S1	10	10	10	1	1
S2	10	01	10	0	1
S3	11	00	10	1	1
S4	01	10	01	0	1
S5	10	10	10	1	0


4. Design the state diagram and control path for programmable data path given in Q No.3 to perform any of (a) Multiplication (b) Division (c) Square root (d) factorial

Multiplication -- Pseudocode

```

p = 0;
while (b >= 1) {
    p = p + a;
    b = b - 1;
}

```

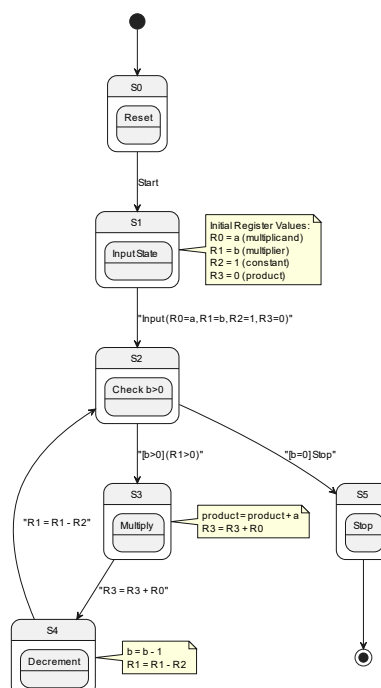State Diagram

Control Signal

State	a_sel	b_sel	op_sel	wsel	wen
S0	10	10	10	1	1
S1	10	10	10	1	1
S2	10	01	10	0	1
S3	11	00	00	1	1
S4	01	10	01	0	1
S5	10	10	10	1	0


Division -- Pseudocode

```

q = 0;
r = a;
while (r >= b) {
    r = r - b;
    q = q + 1;
}

```

State Diagram

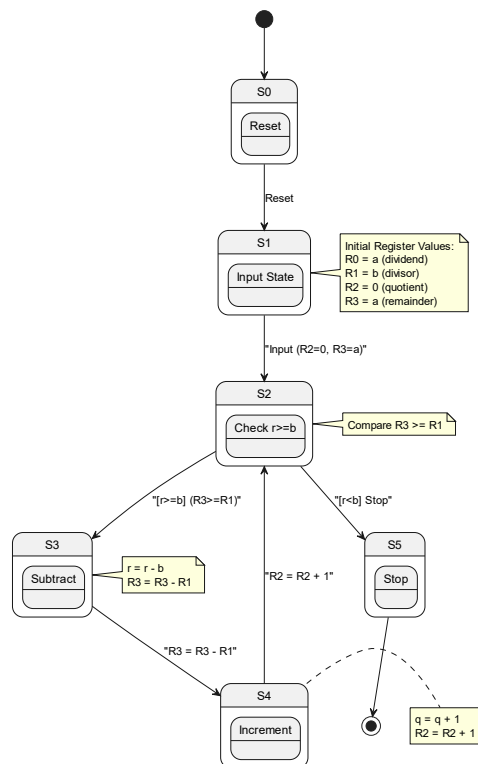

Control Signal

State	a_sel	b_sel	op_sel	wsel	wen
S0	10	10	10	1	1
S1	10	10	10	1	1
S2	10	01	10	0	1
S3	11	00	01	1	1
S4	01	10	00	0	1
S5	10	10	10	1	0


Square root -- Pseudocode

```

r = 0;
temp = a;
count = 1;
while (temp >= count) {
    temp = temp - count;
    count = count + 2;
    r = r + 1;
}

```

State Diagram

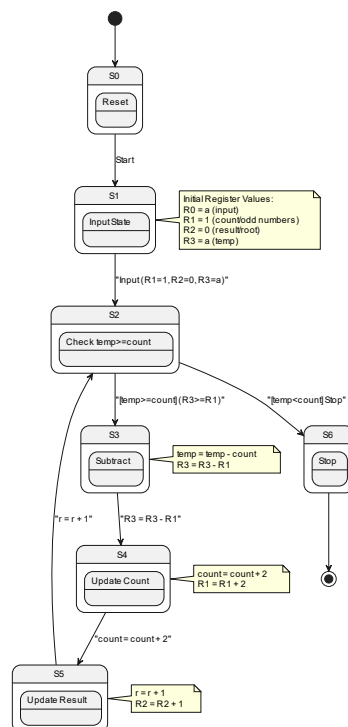

Control Signal


State	a_sel	b_sel	op_sel	wsel	wen
S0	10	10	10	1	1
S1	10	10	10	1	1
S2	10	01	10	0	1
S3	11	00	01	1	1
S4	01	10	00	1	1
S5	01	10	00	0	1
S6	10	10	10	1	0

Factorial -- Pseudocode

```

f = 1;
t = n;
while (t >= 1) {
    f = f * t;
    t = t - 1;
}

```

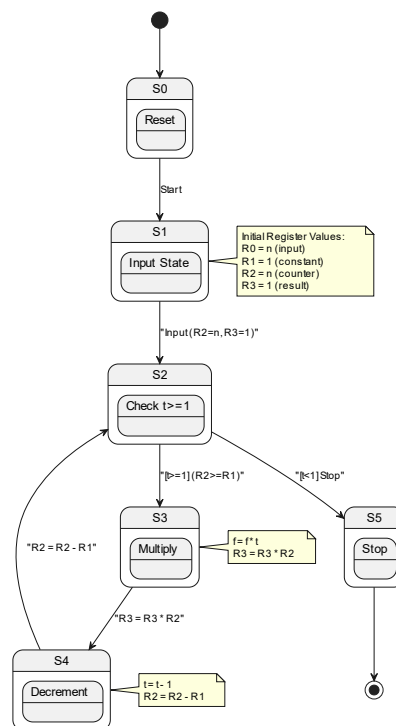State Diagram

Control Signal

State	a_sel	b_sel	op_sel	wsel	wen
S0	10	10	10	1	1
S1	10	10	10	1	1
S2	10	01	10	0	1
S3	11	00	10	1	1
S4	01	10	01	0	1
S5	10	10	10	1	0