

EXPERIMENT- 7

Design and Verilog modeling of Euclid GCD Algorithm

Objective:

Design and Verilog modeling of datapath and control path of GCD algorithm using any modeling style.

Exercise Problems

- 1. Design a datapath for dividing two numbers input by the user, using adder/subtraction, comparator units. Identify the high-level state diagram for the machine.**

Source Code

```
module Division (  
    input clk, rst, start,  
    input [7:0] dividend, divisor,  
    output [7:0] quotient, remainder,  
    output done  
);  
    wire load_dividend, load_divisor, load_quotient, subtract;  
    wire div_geq_div;  
    DP dp (  
        .clk(clk), .rst(rst),  
        .dividend_in(dividend), .divisor_in(divisor),  
        .load_dividend(load_dividend), .load_divisor(load_divisor),  
        .load_quotient(load_quotient), .subtract(subtract),  
        .quotient(quotient), .remainder(remainder),  
        .div_geq_div(div_geq_div), .done(done)  
    );  
    CP cp (  
        .clk(clk), .rst(rst), .start(start),  
        .div_geq_div(div_geq_div),  
        .load_dividend(load_dividend), .load_divisor(load_divisor),  
        .load_quotient(load_quotient), .subtract(subtract),  
        .done(done)  
    );  
endmodule
```

```
module CP (
    input clk, rst, start,
    input div_geq_div,
    output reg load_dividend, load_divisor, load_quotient,
    output reg subtract, done
);
parameter IDLE = 3'b000, LOAD = 3'b001, COMPARE = 3'b010,
           SUBTRACT = 3'b011, DONE = 3'b100;

reg [2:0] state, next_state;
always @(posedge clk or posedge rst)
begin
    if (rst)
        state <= IDLE;
    else
        state <= next_state;
end
always @(posedge clk)
begin
    load_dividend = 0;
    load_divisor = 0;
    load_quotient = 0;
    subtract = 0;
    done = 0;
    case (state)
        IDLE:
            begin
                if (start)
                    next_state = LOAD;
                else
                    next_state = IDLE;
            end
        LOAD:
            begin
                load_dividend = 1;
                load_divisor = 1;
                load_quotient = 1;
                next_state = COMPARE;
            end
        COMPARE:
            begin
                if (div_geq_div)
```

```
        next_state = SUBTRACT;
    else
        next_state = DONE;
    end
    SUBTRACT:
    begin
        subtract = 1;
        next_state = COMPARE;
    end
    DONE:
    begin
        done = 1;
        next_state = IDLE;
    end
    default:
        next_state = IDLE;
    endcase
end

endmodule

module DP (
    input clk, rst,
    input [7:0] dividend_in, divisor_in,
    input load_dividend, load_divisor, load_quotient,
    input subtract,
    input done,
    output reg [7:0] quotient,
    output reg [7:0] remainder,
    output reg div_geq_div
);
    reg [7:0] dividend, divisor;
    always @(posedge clk or posedge rst)
    begin
        if (rst)
        begin
            dividend <= 8'b0;
            divisor <= 8'b0;
            quotient <= 8'b0;
            remainder <= 8'b0;
        end
        else
        begin
```

```
    if (load_dividend)
        dividend <= dividend_in;
    if (load_divisor)
        divisor <= divisor_in;
    if (load_quotient)
        quotient <= 8'b0;
end
end
always @(*)
begin
    div_geq_div = (dividend >= divisor);
end
always @(posedge clk)
begin
    if (subtract && div_geq_div)
    begin
        dividend <= dividend - divisor;
        quotient <= quotient + 1;
    end
    if (done==1)
        remainder <= dividend;
end
endmodule
```

Test-bench

```
module tb();
    reg clk, rst, start;
    reg [7:0] dividend, divisor;
    wire [7:0] quotient, remainder;
    wire done;
    Division uut (
        .clk(clk),
        .rst(rst),
        .start(start),
        .dividend(dividend),
        .divisor(divisor),
        .quotient(quotient),
        .remainder(remainder),
        .done(done)
    );
    initial
```


```
begin
    clk = 0;
    forever
        #10 clk = ~clk;
end
initial
begin
    rst = 1;
    start = 0;
    dividend = 8'b0;
    divisor = 8'b0;
    #20;
    rst = 0;
    dividend = 8'd20;
    divisor = 8'd4;
    start = 1;
    #20 start = 0;
    wait(done);
    #10;
    $display("Test Case 1: 20 / 4 = %d R %d", quotient, remainder);
    if (quotient != 5 || remainder != 0)
        $display("Error: Expected Quotient = 5, Remainder = 0");
    dividend = 8'd25;
    divisor = 8'd4;
    start = 1;
    #20 start = 0;
    wait(done);
    #10;
    $display("Test Case 2: 25 / 4 = %d R %d", quotient, remainder);
    if (quotient != 6 || remainder != 1)
        $display("Error: Expected Quotient = 6, Remainder = 1");
    dividend = 8'd5;
    divisor = 8'd10;
    start = 1;
    #20 start = 0;
    wait(done);
    #10;
    $display("Test Case 3: 5 / 10 = %d R %d", quotient, remainder);
    if (quotient != 0 || remainder != 5)
        $display("Error: Expected Quotient = 0, Remainder = 5");
    dividend = 8'd15;
    divisor = 8'd1;
```

```

start = 1;
#20 start = 0;
wait(done);
#10;
$display("Test Case 4: 15 / 1 = %d R %d", quotient, remainder);
if (quotient != 15 || remainder != 0)
    $display("Error: Expected Quotient = 15, Remainder = 0");
$finish;
end
endmodule

```

Waveform

 


Console

```


ncsim>
ncsim> source /home/install/INCISIVE152/tools/inca/files/ncsimrc
ncsim> run
database -open waves -into waves.shm -default
probe -create -shm tb.clk tb.dividend tb.divisor tb.done tb.quotient tb.remainder tb.rst tb.start
run
Created default SHM database waves
ncsim> Created probe 1
ncsim> Test Case 1: 20 / 4 = 5 R 0
Test Case 2: 25 / 4 = 6 R 1
Error: Expected Quotient = 6, Remainder = 1
Test Case 3: 5 / 10 = 0 R 1
Error: Expected Quotient = 0, Remainder = 5
Test Case 4: 15 / 1 = 15 R 0
Error: Expected Quotient = 15, Remainder = 0
Simulation complete via $finish(1) at time 2660 NS + 0
./lqtb.v:58 $finish;\r
ncsim>

```

Schematic

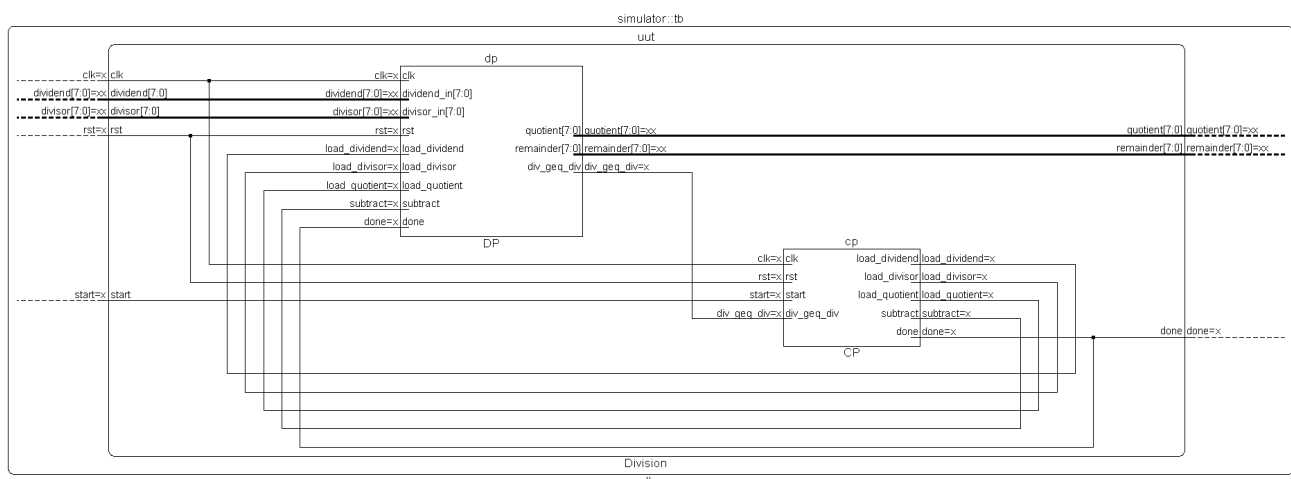

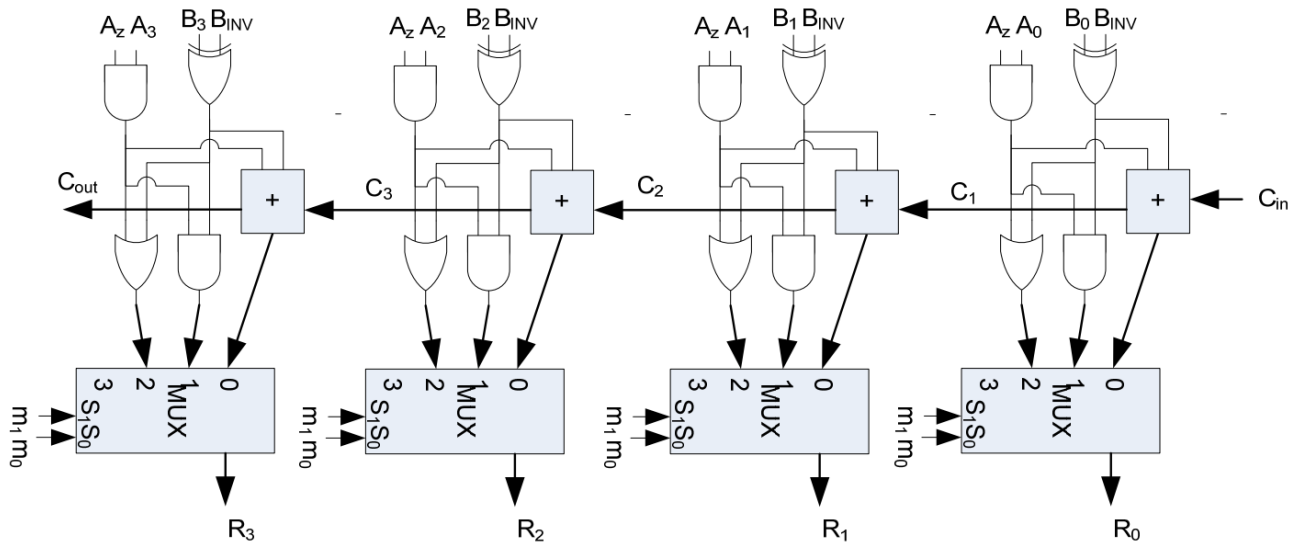2. A 4-bit ALU datapath is given below which can perform the following 5 operations: add, sub, AND, OR and negate B. Inputs are given by $A=\{A_3,A_2,A_1,A_0\}$, $B=\{B_3,B_2,B_1,B_0\}$, and C_{in} . Outputs are result $R=\{R_3,R_2,R_1,R_0\}$ and C_{out} . Numbers are represented in 2's complement form. Design and implement an optimized hardware for the datapath.



Source Code

```
module alu_fsm(reset, a, b, cin, out, sel, cout);
    input reset;
    input [3:0] a, b;
    input cin;
    input [2:0] sel;
    output reg [4:0] out;
    output cout;
    parameter S1 = 3'b000;
    parameter S2 = 3'b001;
    parameter S3 = 3'b010;
    parameter S4 = 3'b011;
    parameter S5 = 3'b100;
    parameter S6 = 3'b101;
    reg [2:0] c_state, n_state;
    reg r1, r2, r3, r4;
    always @(*)
    begin
        if (reset)
            c_state <= S6;
        else
```

```
        c_state <= n_state;
end
always @(*)
begin
    case (sel)
        3'b000:
            n_state <= S1;
        3'b001:
            n_state <= S2;
        3'b010:
            n_state <= S3;
        3'b011:
            n_state <= S4;
        3'b100:
            n_state <= S5;
        default:
            n_state <= S6;
    endcase
end
always @(*)
begin
    case (c_state)
        S1:
            begin
                out <= a+b;
            end
        S2:
            begin
                out <= a-b;
            end
        S3:
            begin
                out <= a&b;
            end
        S4:
            begin
                out <= a|b;
            end
        S5:
            begin
                out <= ~b+1;
            end
    end
```




```
        S6:
        begin
            out <= 5'bxxxx;
        end
    endcase
end
assign cout=out[4];
endmodule
```


Test-bench

```
module tb();
    reg reset;
    reg [3:0] a, b;
    reg cin;
    reg [2:0] sel;
    wire [4:0] out;
    wire cout;
    alu_fsm uut(reset, a, b, cin, out, sel, cout);
    initial
    begin
        reset=1;
        #10 reset=0;
        a=4'b0101;
        b=4'b1100;
        cin=0;
        sel=2'bxx;
        #10 sel=2'b00;
        #10 sel=2'b01;
        #10 sel=2'b10;
        #10 sel=2'b11;
    end
    initial
    begin
        $display("reset=%d, a=%d, b=%d, cin=%d,
sel=%d,out=%d,cout=%d",reset,a,b,cin,sel,out,cout);
    end
    initial
    begin
        #100 $finish();
    end
endmodule
```

Waveform

 

Schematic

 

3. Design a datapath and control unit required to implement the function $F = (a*b)/(c*d)$ using a single programmable (general purpose) datapath using ALU, any number of Registers, Multiplexers, buses etc.

Source Code

```
module datapath(out, sel, ldA, ldB, ldC, ldD, ld0, opsel, clk, a, b, c,
d);
    input sel, ldA, ldB, ldC, ldD, ld0, opsel, clk;
    output [31:0] out;
    input [15:0] a, b, c, d;
    wire [15:0] x, y, ra, rb;
    wire [31:0] rc, rd;
    wire [31:0] m, n, opout;
    MUX m1 (x, sel, a, c, clk);
    MUX m2 (y, sel, b, d, clk);
    MUX1 m3 (opout, opsel, m, n, clk);
    REG1 r1 (ra, ldA, x, clk);
    REG1 r2 (rb, ldB, y, clk);
    REG2 r3 (rc, ldC, opout, clk);
    REG2 r4 (rd, ldD, opout, clk);
    REG2 r5 (out, ld0, opout, clk);
    MUL alu0 (m, ra, rb);
    DIV alu1 (n, rc, rd);
endmodule
```

```
module MUX (dout, sel, in1, in2, clk);
    input [15:0] in1, in2;
    input sel, clk;
    output reg [15:0] dout;
    always@(posedge clk)
    begin
        if(sel == 0)
            dout <= in1;
        else
            dout <= in2;
        end
    endmodule

module MUX1 (dout, sel, in1, in2, clk);
    input [31:0] in1, in2;
    input sel, clk;
    output reg [31:0] dout;
    always@(posedge clk)
    begin
        if(sel == 0)
            dout <= in1;
        else
            dout <= in2;
        end
    endmodule

module REG1 (dout, ld, din, clk);
    input ld, clk;
    input [15:0] din;
    output reg [15:0] dout;
    always@(posedge clk)
    begin
        if(ld)
            dout <= din;
        end
    endmodule

module REG2 (dout, ld, din, clk);
    input ld, clk;
    input [31:0] din;
    output reg [31:0] dout;
    always@(posedge clk)
    begin
        if(ld)
            dout <= din;
        end
    endmodule
```

```
    end
endmodule
module MUL (dout, in1, in2);
    input [15:0] in1, in2;
    output reg [31:0] dout;
    always@(*)
    begin
        dout = in1 * in2;
    end
endmodule
module DIV (dout, in1, in2);
    input [31:0] in1, in2;
    output reg [31:0] dout;
    always@(*)
    begin
        dout = in1 / in2;
    end
endmodule
module controller (sel, ldA, ldB, ldC, ldD, ld0, opsel, done, start,
clk);
    input start, clk;
    output reg sel, ldA, ldB, ldC, ldD, ld0, opsel, done;
    reg [3:0] state;
    parameter s0 = 4'd0,
               s1 = 4'd1,
               s2 = 4'd2,
               s3 = 4'd3,
               s4 = 4'd4,
               s5 = 4'd5,
               s6 = 4'd6,
               s7 = 4'd7,
               s8 = 4'd8,
               s9 = 4'd9;

    always@(posedge clk)
    begin
        case(state)
            s0:
                if(start)
                    state <= s1;
            s1:
                state <= s2;
```

```
s2:
    state <= s3;
s3:
    state <= s4;
s4:
    state <= s5;
s5:
    state <= s6;
s6:
    #10 state <= s7;
s7:
    state <= s8;
s8:
    state <= s9;
s9:
    state <= s9;
default:
    state <= s0;
endcase
end
always@(state)
begin
    case(state)
        s0:
            begin
                #1 ldA = 0;
                ldB= 0;
                ldC = 0;
                ldD = 0;
                ld0 = 0;
                opsel = 0;
                sel = 0;
            end
        s1:
            begin
                #1 sel = 0;
                ldA = 1;
                ldB = 1;
                opsel = 0;
            end
        s2:
            begin
```

```
#1 opsel = 0;
ldA = 0;
ldB = 0;
end
s3:
begin
    #1 ldC = 1;
end
s4:
begin
    #1 ldC = 0;
    sel = 1;
    ldA = 1;
    ldB = 1;
end
s5:
begin
    #1 opsel = 0;
end
s6:
begin
    #1 ldD = 1;
end
s7:
begin
    #1 opsel = 1;
    ldD = 0;
end
s8:
begin
    #1 ldO = 1;
    opsel = 0;
end
s9:
begin
    #1 done = 1;
    ldA = 0;
    ldB = 0;
    ldC = 0;
    ldD = 0;
    ldO = 0;
    opsel = 0;
```

```
    end
    default:
    begin
        ldA = 0;
        ldB= 0;
        ldC = 0;
        ldD = 0;
        ld0 = 0;
        opsel = 0;
        sel = 0;
        done = 0;
    end
endcase
end
endmodule
```

Test-bench


```
module tb();
    reg clk, start;
    wire sel, ldA, ldB, ldC, ldD, ld0, opsel, done;
    reg [15:0] a, b, c, d;
    wire [31:0] out;
    datapath DP (out, sel, ldA, ldB, ldC, ldD, ld0, opsel, clk, a, b, c,
d);
    controller CON (sel, ldA, ldB, ldC, ldD, ld0, opsel, done, start, clk);
    initial
    begin
        clk = 0;
        #3 start = 1;
        forever
            #5 clk = ~clk;
    end
    initial
    begin
        a = 16'd10;
        b = 16'd20;
        c = 16'd1;
        d = 16'd5;
        #300 $finish;
    end
end
```

```

initial
begin
    $monitor("Time: %0d, Output: %d, Done: %b", $time, out, done);
end
endmodule

```

Waveform

 

Console

```

ncsim>
ncsim> source /home/install/INCISIVE152/tools/inca/files/ncsimrc
ncsim> run
database -open waves -into waves.shm -default
probe -create -shm tb.a tb.b tb.c tb.clk tb.d tb.done tb.ldA tb.ldB tb.ldC tb.ldD tb.ld0 tb.opsel tb.out tb.sel tb.start
run
Created default SHM database waves
ncsim> Created probe 1
ncsim> Time: 0, Output:      x, Done: x
Time: 108, Output:      40, Done: x
Time: 109, Output:      40, Done: 1
Simulation complete via $finish(1) at time 300 NS + 0
./3qtb.v:21      #300 $finish;
ncsim>

```

Schematic

