

EXPERIMENT- 3

Verilog Structural Modeling

Objective:

To understand the concepts related to structural modeling style and write Verilog programs using the same.

Theory: Structures can be described in Verilog HDL using

- i. Built in gate primitives (at the gate level) [Note-will be used in this Lab]
- ii. Switch level primitives (at the transistor level)
- iii. User defined primitives (at the gate level)
- iv. Module primitives (to create hierarchy) [Note-will be used in this Lab]

A module can be instantiated in another module, thus creating hierarchy. A module instantiation statement is of the form:

```
Module_name instance_name ( port_association);
```

Port association can be by position or by name, however associations cannot be mixed.

A port association is of the form.

```
port_expr  
    .portname(port_expr)
```

In positional association, the port expressions connect to the ports of the module in the specified order. In association by name, the connection between the module port and the port expression is explicitly specified and thus the order of port associations is not important.

Exercise Problems

- 1. Write structural Verilog code for mod-14 ripple counter and verify the design by simulation.**

Source Code

```
module mod14ripplecounter(input clk,reset,output wire [3:0]q);
TFF tff0(.t(1),.clk(clk),.clear(clr),.reset(reset),.q(q[0]));
TFF tff1(.t(1),.clk(q[0]),.clear(clr),.reset(reset),.q(q[1]));
TFF tff2(.t(1),.clk(q[1]),.clear(clr),.reset(reset),.q(q[2]));
TFF tff3(.t(1),.clk(q[2]),.clear(clr),.reset(reset),.q(q[3]));
and (clr,q[3],q[2],q[1],~q[0]);
endmodule

module TFF(input t,clk,clear,reset,output reg q);
always@(clear)
q<=0;
always @(negedge clk or posedge reset) begin
if (reset)
q <= 0;
else if (t)
q <= ~q;
else
q <= q;
end
endmodule
```

Testbench


```
module tb();
reg clk,reset;
wire [3:0]q;
mod14ripplecounter uut(.clk(clk),.reset(reset),.q(q));
initial begin
clk = 0;
forever #2 clk = ~clk;
end
initial begin
reset = 0;
#2 reset =1;
```

```

#2 reset =0;
#60 reset =1;
#2 reset=0;
#60 $finish;
end
initial begin
$monitor($time, " clk=%b, q=%b",clk,q);
end
endmodule

```

Waveform

 


Console

```

ncsim> run
0 clk=0, q=xxxx
2 clk=1, q=0000
4 clk=0, q=0001
6 clk=1, q=0001
8 clk=0, q=0010
10 clk=1, q=0010
12 clk=0, q=0011
14 clk=1, q=0011
16 clk=0, q=0100
18 clk=1, q=0100
20 clk=0, q=0101
22 clk=1, q=0101
24 clk=0, q=0110
26 clk=1, q=0110
28 clk=0, q=0111
30 clk=1, q=0111
32 clk=0, q=1000
34 clk=1, q=1000
36 clk=0, q=1001
38 clk=1, q=1001
40 clk=0, q=1010
42 clk=1, q=1010
44 clk=0, q=1011
46 clk=1, q=1011
48 clk=0, q=1100
50 clk=1, q=1100
52 clk=0, q=1101
54 clk=1, q=1101
56 clk=0, q=0000
58 clk=1, q=0000
60 clk=0, q=0001
62 clk=1, q=0001
64 clk=0, q=0000
66 clk=1, q=0000
68 clk=0, q=0001
70 clk=1, q=0001
72 clk=0, q=0010
74 clk=1, q=0010
76 clk=0, q=0011
78 clk=1, q=0011
80 clk=0, q=0100
82 clk=1, q=0100
84 clk=0, q=0101
86 clk=1, q=0101
88 clk=0, q=0110
90 clk=1, q=0110
92 clk=0, q=0111
94 clk=1, q=0111
96 clk=0, q=1000
98 clk=1, q=1000
100 clk=0, q=1001
102 clk=1, q=1001
104 clk=0, q=1010
106 clk=1, q=1010
108 clk=0, q=1011
110 clk=1, q=1011
112 clk=0, q=1100
114 clk=1, q=1100
116 clk=0, q=1101
118 clk=1, q=1101
120 clk=0, q=0000
122 clk=1, q=0000
124 clk=0, q=0001
Simulation complete via $finish(1) at time 126 NS + 0
./mod14ripplecounter_tb.v:15 #60 $finish;
ncsim>


```

Schematic

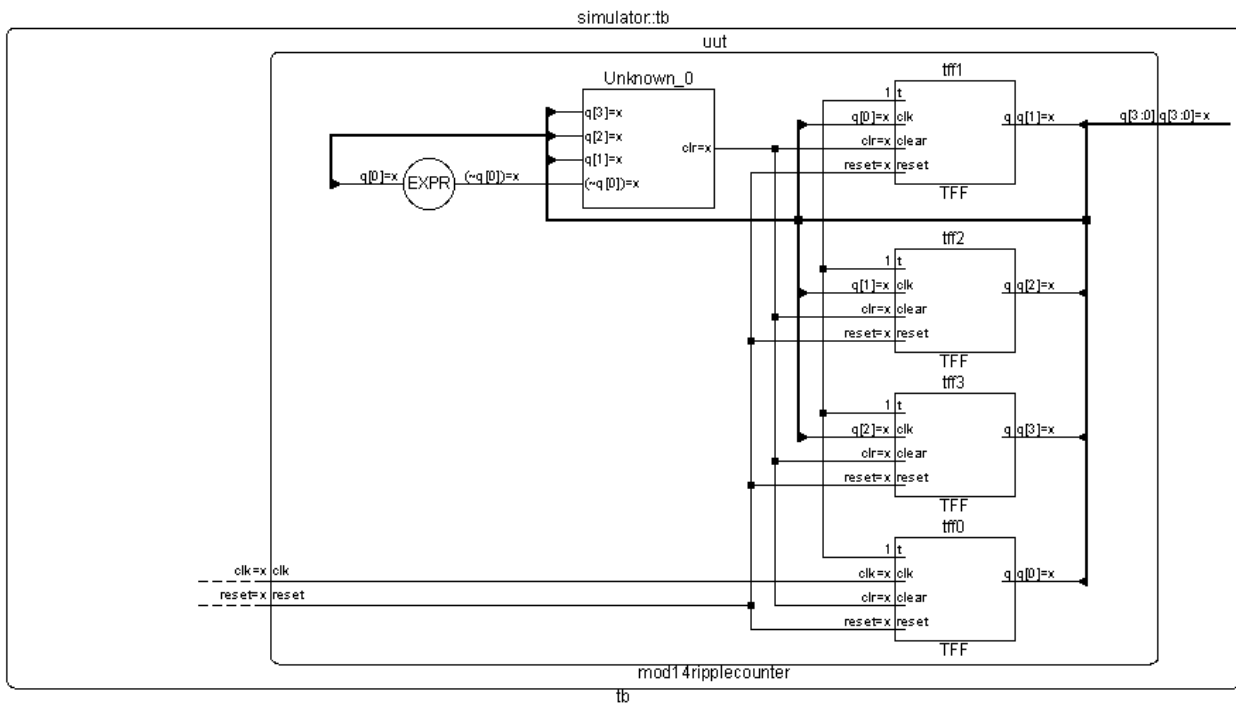

2. Write structural Verilog code for 4-bit carry look ahead adder and verify the design by simulation.

Circuit

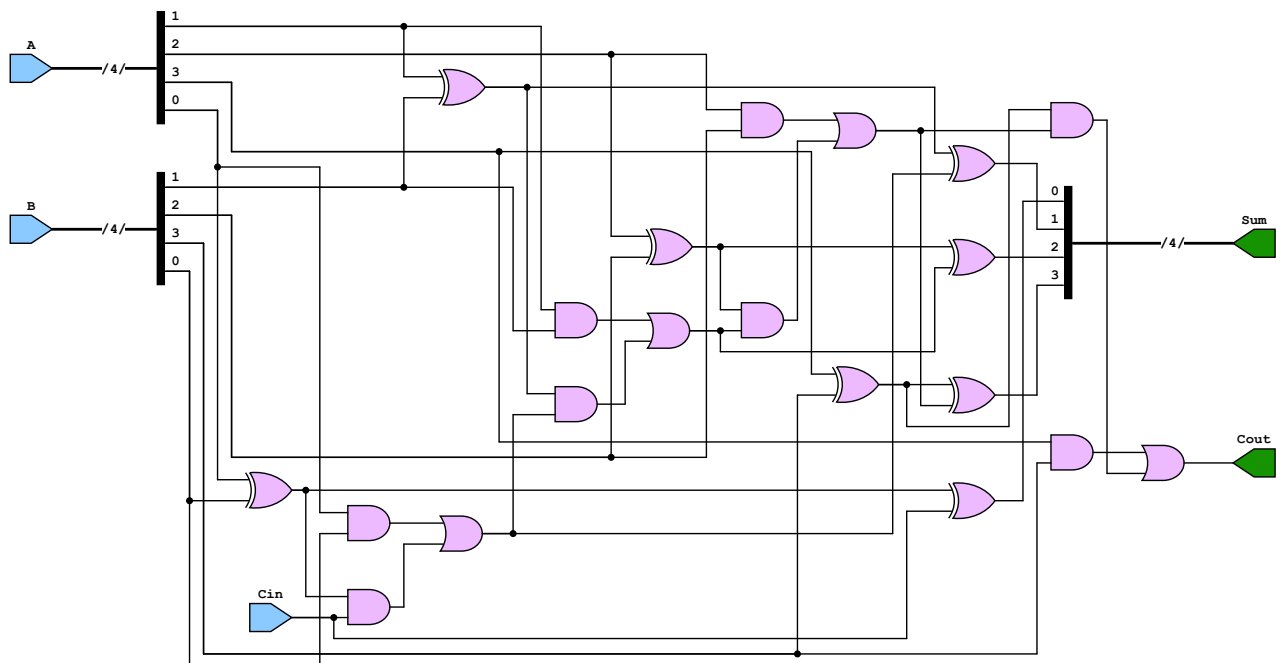

Source Code

```
module claa(input [3:0]A,B,input Cin,output [3:0]Sum,output Cout);
wire [3:0] P, G, C;
wire pp1,pp2,pp3,pp4;
xor (P[0],A[0],B[0]);
xor (P[1],A[1],B[1]);
xor (P[2],A[2],B[2]);
xor (P[3],A[3],B[3]);

and (G[0],A[0],B[0]);
and (G[1],A[1],B[1]);
and (G[2],A[2],B[2]);
and (G[3],A[3],B[3]);

assign C[0] = Cin;

and a1(pp1,P[0],C[0]);
or o1(C[1],G[0],pp1);

and a2(pp2,P[1],C[1]);
or o2(C[2],G[1],pp2);

and a3(pp3,P[2],C[2]);
or o3(C[3],G[2],pp3);

and a4(pp4,P[3],C[3]);
or o4(Cout,G[3],pp4);

xor (Sum[0],P[0],C[0]);
xor (Sum[1],P[1],C[1]);
xor (Sum[2],P[2],C[2]);
xor (Sum[3],P[3],C[3]);

endmodule
```


Testbench

```

module tb();
reg [3:0] A, B;
reg Cin;
wire [3:0] Sum;
wire Cout;
claa uut (.A(A),.B(B),.Cin(Cin),.Sum(Sum),.Cout(Cout));
initial begin
$monitor($time," A:%b,B:%b,Cin:%b,Sum:%b,Cout:%b ",A,B,Cin,Sum,Cout);
A=4'b0000; B=4'b1111; Cin=1;
#10;
A=4'b0011; B=4'b1001; Cin=0;
#10;
A=4'b0110; B=4'b0011; Cin=1;
#10;
A=4'b0101; B=4'b1000; Cin=1;
#10;
A=4'b1111; B=4'b0000; Cin=1;
#10;
$finish;
end
endmodule

```


Waveform

 

Console


```
ncsim>
ncsim> source /home/install/INCISIVE152/tools/inca/files/ncsimrc
ncsim> run
database -open waves -into waves.shm -default
probe -create -shm tb.A tb.B tb.Cin tb.Cout tb.Sum
run
Created default SHM database waves
ncsim> Created probe 1
ncsim>
0 A:0000,B:1111,Cin:1,Sum:0000,Cout:1
10 A:0011,B:1001,Cin:0,Sum:1100,Cout:0
20 A:0110,B:0011,Cin:1,Sum:1010,Cout:0
30 A:0101,B:1000,Cin:1,Sum:1110,Cout:0
40 A:1111,B:0000,Cin:1,Sum:0000,Cout:1
Simulation complete via $finish(1) at time 50 NS + 0
./cla4bit_tb.v:19 $finish;
ncsim>
```

Schematic

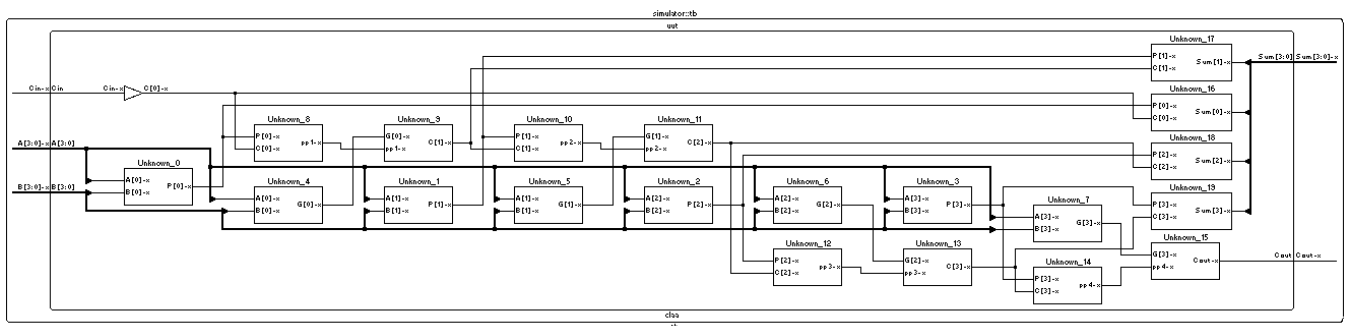

3. Write structural Verilog code for 4-bit carry select adder and verify the design by simulation.

Circuit

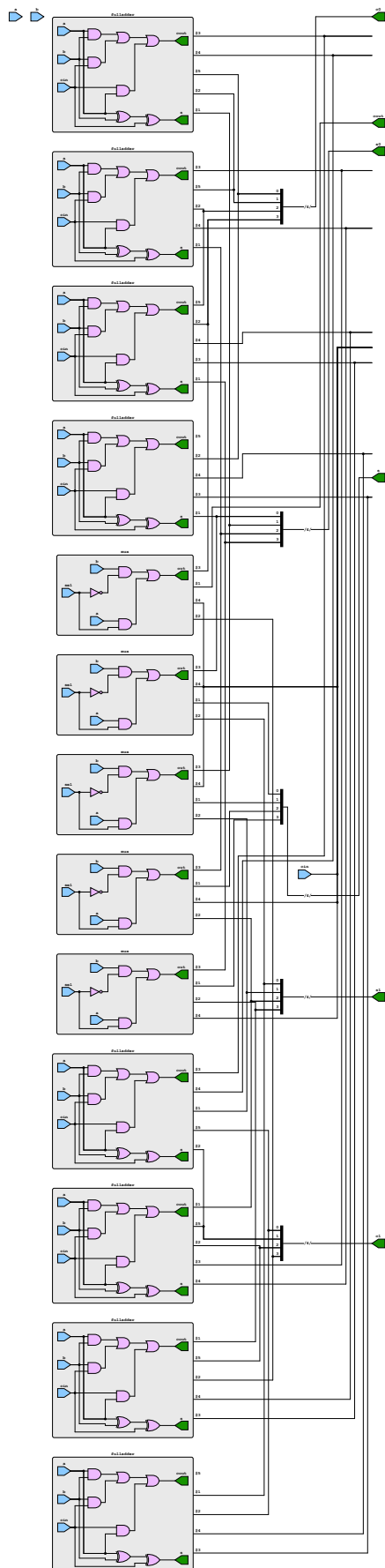

Source Code

```
module carryselect(output [3:0]s,s0,s1,c0,c1,output cout,input
[3:0]a,b,input cin);
```

```
fulladder f0(s0[0],c0[0],a[0],b[0],1'b0);
fulladder f1(s0[1],c0[1],a[1],b[1],c0[0]);
fulladder f2(s0[2],c0[2],a[2],b[2],c0[1]);
fulladder f3(s0[3],c0[3],a[3],b[3],c0[2]);
```

```
fulladder f4(s1[0],c1[0],a[0],b[0],1'b1);
fulladder f5(s1[1],c1[1],a[1],b[1],c1[0]);
fulladder f6(s1[2],c1[2],a[2],b[2],c1[1]);
fulladder f7(s1[3],c1[3],a[3],b[3],c1[2]);
```

```
mux m0(s[0],s1[0],s0[0],cin);
mux m1(s[1],s1[1],s0[1],cin);
mux m2(s[2],s1[2],s0[2],cin);
mux m3(s[3],s1[3],s0[3],cin);
mux m4(cout,c1[3],c0[3],cin);
```

```
endmodule
```

```
module mux(output out,input a,b,sel);
not n1(sel_n,sel);
and a1(sel_b,b,sel_n); //sel=0 out=b
and a2(sel_a,a,sel); //sel=1 out=a
or o1(out,sel_b,sel_a);
endmodule
```

```
module fulladder(output s,cout,input a,b,cin);
xor sum(s,a,b,cin);
and a1(c1,a,b);
and a2(c2,b,cin);
and a3(c3,cin,a);
or carry(cout,c1,c2,c3);
endmodule
```


Testbench

```

module tb();
reg [3:0]a,b;
reg cin;
wire [3:0]s,s0,s1,c0,c1;
wire cout;
carryselect
uut(.s(s),.s0(s0),.s1(s1),.c0(c0),.c1(c1),.cout(cout),.a(a),.b(b),.cin(cin));
initial begin
$monitor($time," a=%b b=%b cin=%b s=%b cout=%b ",a,b,cin,s,cout);
a = 4'b1100; b = 4'b0001; cin = 1'b0;#2;
a = 4'b1100; b = 4'b0001; cin = 1'b1;#2;
a = 4'b1001; b = 4'b0100; cin = 1'b0;#2;
a = 4'b1001; b = 4'b0100; cin = 1'b1;#2;
a = 4'b1111; b = 4'b0001; cin = 1'b0;#2;
a = 4'b1111; b = 4'b0001; cin = 1'b1;#2;
$finish;
end
endmodule

```

Waveform

 


Console

```


ncsim>
ncsim> source /home/install/INCISIVE152/tools/inca/files/ncsimrc
ncsim> run
          0 a=1100 b=0001 cin=0 s=1101 cout=0
          2 a=1100 b=0001 cin=1 s=1110 cout=0
          4 a=1001 b=0100 cin=0 s=1101 cout=0
          6 a=1001 b=0100 cin=1 s=1110 cout=0
          8 a=1111 b=0001 cin=0 s=0000 cout=1
         10 a=1111 b=0001 cin=1 s=0001 cout=1
Simulation complete via $finish(1) at time 12 NS + 0
./carryselect_tb.v:15 $finish;
ncsim>

```

Schematic

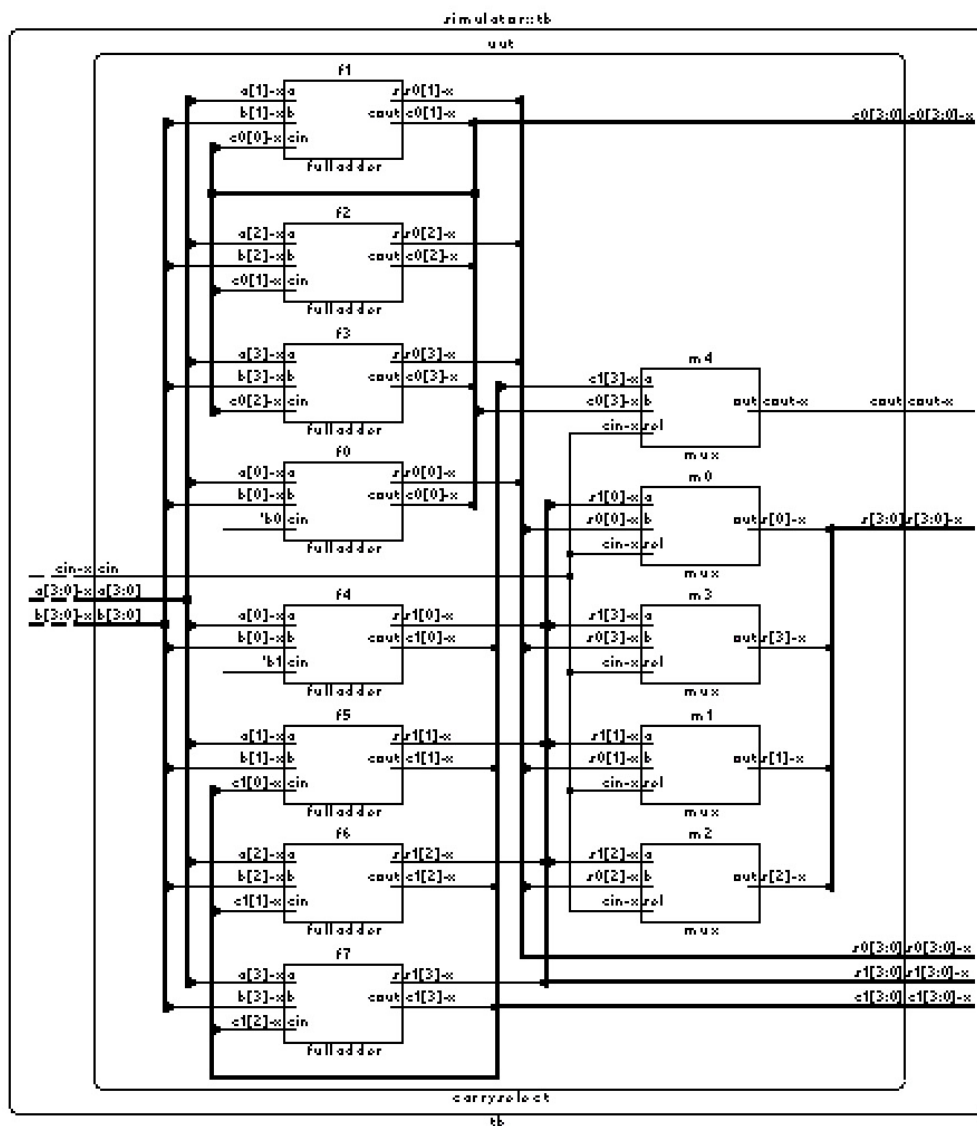

4. Write structural Verilog code for 4-bit carry save adder and verify the design by simulation.

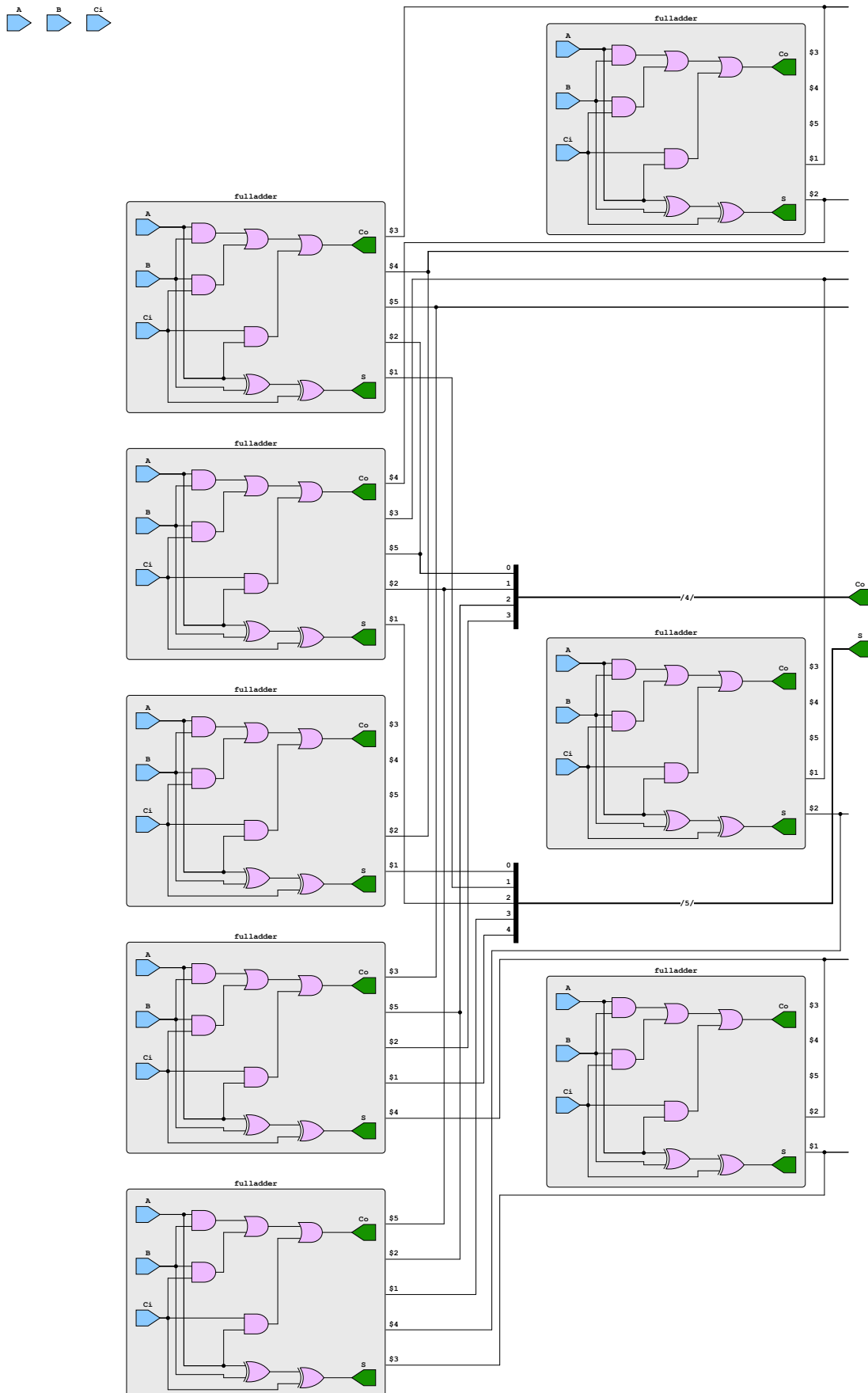Circuit

Source Code


```
module carrysave(output [4:0]S,output [3:0]Co,input [3:0]A,B,Ci);
wire [2:0]Si;
wire [3:0]Cio;
fulladder f0(S[0],Cio[0],A[0],B[0],Ci[0]);
fulladder f1(Si[0],Cio[1],A[1],B[1],Ci[1]);
fulladder f2(Si[1],Cio[2],A[2],B[2],Ci[2]);
fulladder f3(Si[2],Cio[3],A[3],B[3],Ci[3]);
fulladder f4(S[1],Co[0],Si[0],Cio[0],1'b0);
fulladder f5(S[2],Co[1],Si[1],Cio[1],Co[0]);
fulladder f6(S[3],Co[2],Si[2],Cio[2],Co[1]);
fulladder f7(S[4],Co[3],1'b0,Cio[3],Co[2]);
endmodule

module fulladder(output S,Co,input A,B,Ci);
xor sum(S,A,B,Ci);
and a1(c1,A,B);
and a2(c2,B,Ci);
and a3(c3,Ci,A);
or carry(Co,c1,c2,c3);
endmodule
```

Testbench

```
module tb();
wire [4:0]S;
wire [3:0]Co;
reg [3:0]A,B,Ci;
carrysave uut(.S(S),.Co(Co),.A(A),.B(B),.Ci(Ci));
initial begin
$monitor ($time,"a=%b , b=%b , cin=%b ,s=%b ,cout=%b ",A,B,Ci,S,Co);
A=4'b1000; B=4'b0111; Ci=4'b0000; #2
A=4'b0010; B=4'b1011; Ci=4'b0001; #2
A=4'b1010; B=4'b0101; Ci=4'b0000; #2
A=4'b0010; B=4'b1110; Ci=4'b0001; #2
A=4'b0110; B=4'b1001; Ci=4'b0000; #2
$finish;
end
endmodule
```

Waveform

 

Console

```
ncsim>
ncsim> run
database -open waves -into waves.shm -default
probe -create -shm tb.A tb.B tb.Ci tb.Co tb.S
run
Created default SHM database waves
ncsim> Created probe 1
ncsim>
          0a=1000 , b=0111 , cin=0000 , s=01111 , cout=0000
          2a=0010 , b=1011 , cin=0001 , s=01110 , cout=0000
          4a=1010 , b=0101 , cin=0000 , s=01111 , cout=0000
          6a=0010 , b=1110 , cin=0001 , s=10001 , cout=0110
          8a=0110 , b=1001 , cin=0000 , s=01111 , cout=0000
Simulation complete via $finish(1) at time 10 NS + 0
./carrysave_tb.v:13 $finish;
ncsim>
```

Schematic

